

**Code : 15EC31T**

*Register  
Number*

**III Semester Diploma Examination, Nov./Dec.-2018**  
**ANALOG ELECTRONIC CIRCUITS**

**Time : 3 Hours ]**

**[ Max. Marks : 100**

- Instructions :** (1) Answer any **six** questions from Part – A.  
(2) Answer any **seven** full questions from Part – B.


**PART – A**

1. Explain the need for rectifier in DC regulated power supply, sketch the output waveform of half wave rectifier for sine input. 5
2. Describe the working of C-filter with circuit and waveform. 5
3. Define biasing of BJT and explain need for biasing. 5
4. Write a note on ideal characteristics of Op-Amp. 5
5. Explain the block diagram of Op-Amp. 5
6. Describe the working principle of basic differential amplifier circuit. 5
7. Define Active filter and mention its classification. 5
8. Explain positive shunt clipper circuit using diode. 5
9. Explain the role of Tank circuit in an oscillator. 5

## PART – B

10. Define : 10
- (a) Rectification
  - (b) Ripple factor
  - (c) Ripple frequency
  - (d) Efficiency
  - (e) Peak inverse voltage
- with respect to Rectifiers.
11. (a) Illustrate how UPS keeps power supply uninterrupted. 5
- (b) List applications of SMPS and RPS. 5
12. (a) Explain the working of Class B push-pull amplifier. 5
- (b) List the features of RC-coupled amplifier. 5
13. (a) Establish relation between gains of individual stages and overall gain in a multistage amplifier. 5
- (b) Explain the working of class C amplifier. 5
14. Define : 10
- (a) Input offset voltage
  - (b) Power supply rejection ratio
  - (c) CMRR
  - (d) Gain-Bandwidth product
  - (e) Slew rate
- with respect to Op-Amp.

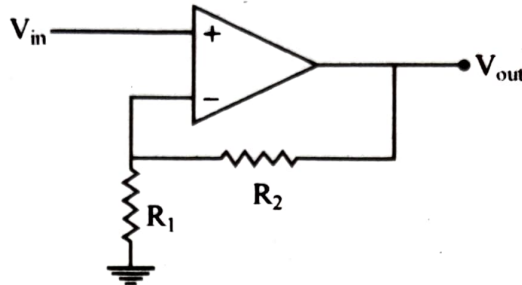15. (a) If  $V_{in} = 2V$ ,  $R_1 = R_2 = 1k\Omega$ , find the output voltage and voltage gain of the following circuit :



5

- (b) Mention the applications of Active Filter.

5

16. Construct first order High Pass Filter with cut-off frequency of 1 kHz and sketch its frequency response and its pass band. Gain is 10.

10

17. (a) Show how Band Elimination Filter can be realized using LPF and HPF.

5

- (b) Mention the applications of PLL.

5

18. Explain the working of simple positive clipper and positive clamper.

10

19. (a) List the expression for oscillating frequency for Hartley, Collpit's, RC-Phase shift and Wien Bridge oscillator.

8

- (b) State Barkhausen criterion.

2