

1289**Code : 15EC33T**Register
Number


--	--	--	--	--	--	--

III Semester Diploma Examination, April/May-2018**ANALOG COMMUNICATION****Time : 3 Hours]****[Max. Marks : 100**

- Note :** (i) Answer any **six** full questions from Part – A
(ii) Answer any **seven** full questions from Part – B

PART – A**(Answer any six questions from Part-A)**

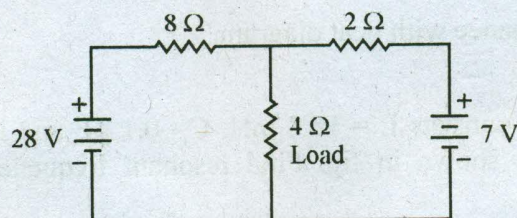1. State and explain maximum power transfer theorem.
2. Draw the Norton's equivalent circuit for the network shown in the figure across $4\ \Omega$ load.




3. Derive an expression for resonant frequency for a series resonant circuit. 5
4. Write a note on attenuators. 5
5. Explain co-axial cable with diagram. 5
6. Define reflection co-efficient and standing wave ratio. 5
7. Explain the working principle of parabolic reflector with suitable diagram. 5
8. Explain ground wave propagation. 5
9. Write a note on VSB and mention its advantages and disadvantages. 5

PART – B

(Answer any seven full questions from Part-B)

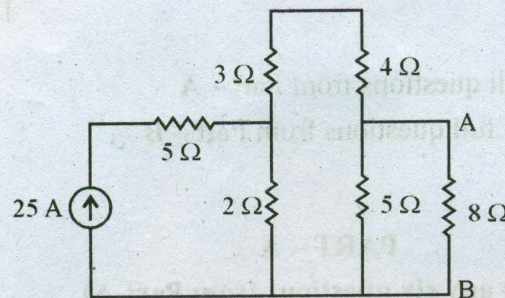
10. State Thevenin's theorem. Write the steps to reduce any linear internal network into its equivalent Thevenin's network. 10
11. Using Norton's theorem find current through 8Ω resistor for the circuit shown in figure. 10



BETA CONSOLE!

Diploma - [All Branches]

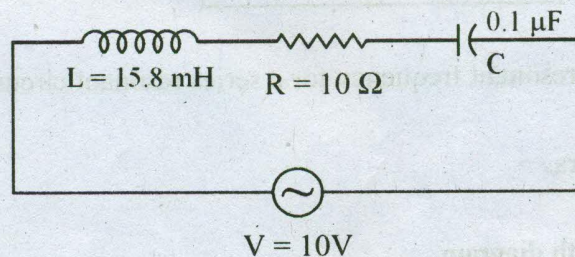12. (a) Design constant KT type LPF with cut-off frequency 4 KHz and characteristics impedance of 600Ω . 5
- (b) Explain parallel resonance with neat diagram. 5
13. (a) A series RLC circuit consists $L = 15.8\text{ mH}$, $C = 0.1\text{ }\mu\text{F}$ and $R = 10\Omega$ and line voltage $V = 10\text{V}$ as shown in fig. Find resonant frequency and current at resonance. 5



- (b) Mention the applications of attenuator. 5
14. Explain the need of impedance matching in a transmission line. Discuss single stub and double stub matching in a line. 10
15. (a) Write features of the Yagi – Uda antenna. 5
- (b) Define polarization and isotropic radiators, directivity, power gain, and antenna resistance. 5

16. (a) Derive the expression for AM waves. 5
(b) Explain the need of modulation. 5
17. (a) Explain the working of linear diode detector circuit with the help of waveform. 5
(b) Write a short note on SSBSC. 5
18. (a) State the demerits of FM over AM. 5
(b) Write a note on pre-emphasis and de-emphasis. 5
19. (a) Explain the Foster – Seeley method of FM detection. 5
(b) Write a note on Ratio detector. 5
-

BETA CONSOLE!

Diploma - [All Branches]

Beta Console Education

3+



Diploma Question Papers [2015-19]

Beta Console Education

3+