

**1133****Code : 15EC-33T**

Register Number

--	--	--	--	--	--	--

**III Semester Diploma Examination, April/May-2017****ANALOG COMMUNICATION****Time : 3 Hours ]****[ Max. Marks : 100**

- Note :** (i) Answer any **six** questions from **Part-A**.  
(ii) Answer any **seven** full questions from **Part-B**.


**PART – A**

1. State and explain Superposition theorem. 5
2. State the Norton's theorem and write the steps to solve the network using Norton's theorem. 5
3. Derive an expression for series resonant frequency. 5
4. Define filter, and give the classification of filters. 5
5. What are the primary and secondary constants of transmission line ? 5
6. Write a note on Single-stub matching and double-stub matching. 5
7. Explain briefly the working of broadside antenna array. 5
8. Write two merits and three demerits of ground wave propagation. 5
9. Explain the Electronic communication system with Block diagram. 5

**PART – B**

10. Find the current through  $4\Omega$  resistor, using Thevenin's theorem.

10

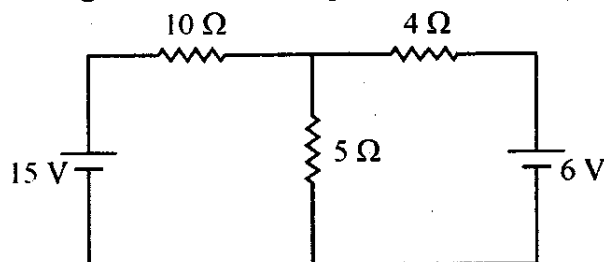

11. Illustrate the application of maximum power transfer theorem with an Example.

10

12. Derive expression for frequency of resonance, Q factor, power factor and Band width & selectivity, for parallel resonance.

10

13. Design a symmetrical T-type and  $\pi$ -type attenuator whose attenuation factor of 30 dB and characteristic resistance is  $600\Omega$  and sketch the ckt's.

BETA CONSOLE!

14. What are transmission lines ? Mention their classification and Explain any one of them with a neat figure.

Diploma - [All Branches]  
Beta Console Education

10

15. (a) Explain briefly the working of end fire array.  
(b) Explain the working of parabolic reflector.

5

Diploma Question Papers [2015-19]  
Beta Console Education

16. (a) Explain the need for modulation and list the modulation techniques.  
(b) Explain AM linear diode detector circuit.

5

5

17. Explain the working principle of

- (a) SSBSC  
(b) DSBSC

5

5

18. (a) Explain the working of varactor diode method of FM generation.  
(b) Write note on Pre-emphasis and De-emphasis circuits.

5

5

19. Explain the Foster-Seeley method of FM detection with a, neat diagram.

10