

1191**Code : 15EC31T**

Register
Number

--	--	--	--	--	--	--

III Semester Diploma Examination, Nov./Dec. 2017
ANALOG ELECTRONICS CIRCUITS

Time : 3 Hours |**| Max. Marks : 100**

- Note :** (i) Answer any **SIX** Questions from **PART-A**. ($5 \times 6 = 30$ marks)
(ii) Answer any **SEVEN** full Questions from **PART-B**. ($7 \times 10 = 70$ marks)

PART-A

1. Define regulator & explain the need for voltage regulators in power supplies. **5**
2. Show mathematically the ripple factor of a bridge rectifier is 0.48. **5**
3. Define Amplification, gain, frequency response, bandwidth & Li/P impedance as applicable to amplifier. **5**
4. Explain the principle of transistor as an amplifier. **5**
5. List the applications of op-amp. **5**
6. Sketch op-amp. voltage follower ckt. & explain it. **5**
7. Define active filter & mention its classification. **5**
8. Compare clipper & clamping circuit. **5**
9. Discuss the role of tank circuit in oscillator circuit. **5**

PART-B

10. Define UPS. With a neat block diagram explain the working principle of online & offline UPS. 10
11. (a) Explain the operation of center tapped full wave rectifier with W/F's. 5
 (b) Explain the SMPS with a neat block diagram. 5
12. (a) Define operating pt & describe the role of DC load line to locate it. 5
 (b) Explain the working of class-A series fed amplifier. 5
13. (a) Establish a relationship between gains of individual stages & overall gain in a multistage amplifier. 5
 (b) List the features of RC coupled amplifier. 5
14. (a) Define the following terms with reference to op-amp. 5
 (i) O/P offset voltage
 (ii) CMRR
 (iii) O/P impedance
 (iv) Gain
 (v) Slew rate
 (b) Construct and label an inverting amplifier ckt. for a voltage gain of 10. 5
15. (a) Construct Schmitt trigger ckt using op-amp. 5
 (b) Demonstrate how op-amp can be used as a differentiator. 5
16. (a) Describe the operation of PLL & its applications. 5
 (b) Describe a first order butterworth LPF ckt for a gain of 10 & cut off frequency of 160 Hz. 5
17. (a) Explain the working of instrumentation amplifier ckt. 5
 (b) Realize the B.P.F. and B.E.F. using L.P.F. and H.P.F. 5
18. (a) Define clamper. Explain a simple positive clamper ckt. 5
 (b) Explain negative shunt clipper. 5
19. (a) Draw & explain RC phase shift oscillator. 5
 (b) Explain the working of collpitts oscillator. 5

BETA CONSOLE!

Diploma - [All Branches]

Beta Console Education

3+



Diploma Question Papers [2015-19]

Beta Console Education

3+

