

**1007****Code : 9EC31**Register  
Number

--	--	--	--	--	--	--

**III Semester Diploma Examination, Nov./Dec. 2016****ANALOG ELECTRONICS CIRCUITS****Time : 3 Hours ]****[ Max. Marks : 100**

- Note :** (i) Question No. 1 is *compulsory*.  
(ii) Answer any **two** full questions from the each remaining sections.

1. (a) Fill in the blanks : 5
- (i) Integrator is also referred as \_\_\_\_\_.
  - (ii) In open loop configuration the gain of the Op-Amp is \_\_\_\_\_.
  - (iii) PLL stands for \_\_\_\_\_.
  - (iv) Gain is expressed in terms of \_\_\_\_\_.
  - (v) Output frequency present in the rectifiers is called \_\_\_\_\_.
- (b) Explain Schmitt trigger circuit with neat diagram. 5

**BETA CONSOLE****SECTION – A**

2. (a) With a neat diagram, explain the operation of bridge rectifier. 6
- (b) With a neat block diagram explain the regulated power supply. 5
- (c) Define load and line regulation. 4
3. (a) With the help of block diagram explain the operation of online UPS. 8
- (b) Explain the working of monostable multivibrator using IC-555. 7
4. (a) What is Barkhausen criteria ? Explain. 5
- (b) Explain the concept of positive feedback. 4
- (c) With a neat block diagram explain Wein bridge oscillator. 6

**SECTION – B**

5. (a) Explain the working of common emitter RC coupled amplifier with its frequency response.  
(b) Define stability factor of common emitter circuit.  
(c) Define the following w.r.t. amplifiers :  
(i) AC load line  
(ii) DC load line  
(iii) Operating point
6. (a) Compare Class 'A', Class 'B' and Class 'C' power amplifiers. (Any three)  
(b) With a neat block diagram explain the operation of class 'B' push-pull amplifier.  
(c) Explain the working of combinational clipper circuit.
7. (a) What is clamper ? Explain +ve clamper circuit with waveforms.  
(b) Explain the working of RC Integrator.  
(c) List the applications of clippers and clampers.

**SECTION – C**

8. (a) Explain the operation of PLL with neat block diagram.  
(b) Explain with a circuit, Op-Amp as summing amplifier.  
(c) List the ideal characteristics of Op-Amp.
9. (a) Explain the working of Non-Inverting amplifiers and obtain the expression for voltage gain.  
(b) Define CMRR.  
(c) Write a short note on notch filter.
10. (a) Explain the voltage to frequency converter circuit.  
(b) Explain Instrumentation amplifier using Op-Amp.  
(c) Explain the concept of virtual ground.
-