

1131

Code : 15EC-31

Register Number

--	--	--	--	--	--	--

III Semester Diploma Examination, April/May-2017
ANALOG ELECTRONICS CIRCUITS

Time : 3 Hours |

| Max. Marks : 100

- Note :** (i) Answer any **SIX** questions from **Part-A**.
(ii) Answer any **SEVEN** full questions from **Part-B**.


PART - A

- | | |
|---|---|
| 1. Explain the working of ON-Line UPS. | 5 |
| 2. Sketch and explain full wave Centre tapped rectifier circuit. | 5 |
| 3. Define biasing of BJT and explain the need for biasing. | 5 |
| 4. Explain the operation of transformer coupled class-A power amplifier. | 5 |
| 5. Explain the block diagram of OP-amp. | 5 |
| 6. List any 5 ideal characteristics of OP-amp. | 5 |
| 7. List any 5 advantages of active filter over passive filters. | 5 |
| 8. Explain the operation of positive clamper circuit. | 5 |
| 9. Describe how oscillations develop in LC tank circuit with a suitable sketch. | 5 |

PART - B

- | | |
|---|---|
| 10. (a) Describe the block diagram of regulated DC power supply. | 5 |
| (b) Show mathematically the ripple factor of a half wave rectifier is 1.21. | 5 |
| 11. (a) Explain the working of π -filter with Half wave rectifier. | 5 |
| (b) Explain IC voltage regulator using LM 317. | 5 |

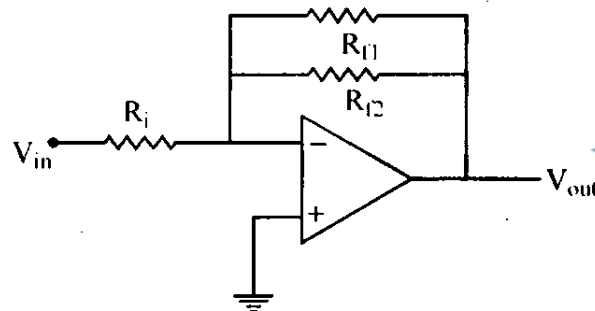12. (a) Explain the concept of AC Load line for large signal amplifiers. **5**
 (b) Describe the working of class-AB amplifier. **5**
13. (a) Explain the working of common emitter RC coupled amplifier. **5**
 (b) Tabulate the efficiencies and conduction angles of power amplifiers. **5**
14. (a) Define the following w.r.t. Op-amp :
 (i) Input offset voltage
 (ii) CMRR
 (iii) Input impedance
 (iv) Slew-rate
 (v) PSRR **5**
 (b) Construct an Op-amp circuit that converts square wave into triangular wave. **5**
15. (a) Explain the working of Schmitt trigger circuit using Op-amp & also sketch the hysteresis plot. **5**
 (b) Estimate the gain in the following circuit given $R_i = 1 \text{ k}\Omega$, $R_{f1} = R_{f2} = 10 \text{ k}\Omega$ **5**



BETA CONSOLE!

Diploma - [All Branches]

Beta Console Education

3+

Diploma Question Papers [2015-19]

Beta Console Education

16. (a) Illustrate how Band elimination filter (BEF) can be realized using LPF & HPF. **7**
 (b) List any 3 applications of active filter. **3**
17. (a) Explain the operation of PLL with a neat diagram. **6**
 (b) Design a first order butter worth LPF circuit for a gain of 10, cut off frequency of 1 kHz. **4**
18. (a) List any 5 applications of clipper circuit. **5**
 (b) Illustrate the operation of RC differentiator with response to square wave signal. **5**
19. (a) Explain the working of wein-bridge oscillator with neat circui diagram. **6**
 (b) A Hartley oscillator circuit has $C = 500 \text{ pf}$, $L_1 = 20 \text{ mH}$ & $L_2 = 5\text{mH}$. Find the
 (i) frequency of oscillation
 (ii) Sketch Hartly oscillator circuit using BJT. **4**