

Register
Number

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

III Semester Diploma Examination, April/May-2019
ANALOG ELECTRONICS CIRCUITS

Time : 3 Hours]

[Max. Marks : 100

- Instructions :** (i) Answer any **six** questions from Part – A. ($6 \times 5 = 30$ marks)
(ii) Answer any **seven** full questions from Part – B. ($7 \times 10 = 70$ marks)

PART – A

1. List any five IC voltage regulators and mention their rated output voltage levels. 5
2. List any five comparison between ON-line and OFF-line UPS. 5
3. Define biasing of BJT and explain the need for biasing. 5
4. Classify the power amplifiers and explain. 5
5. Show mathematically that the gain of a non-inverting amplifier is $1 + \frac{R_f}{R_{in}}$. 5
6. List any five applications of Op-Amp. 5
7. List any five applications of active filters. 5
8. Sketch and explain the combinational clipping circuit. 5
9. Define oscillator. Explain Barkhausen criteria for obtaining sustained oscillation. 5

PART – B

10. (a) Describe the operation of half wave rectifier circuit with waveforms. 6
(b) Show mathematically the ripple factor of a bridge rectifier is 0.48. 4
11. (a) Explain the block diagram of SMPS. 6
(b) Explain voltage regulator using Zener diode. 4
12. (a) Explain the working of a voltage divider bias circuit. 5
(b) List any five differences between Class-A and Class-B power amplifiers. 5
13. (a) Differentiate between voltage and power amplifiers. 4
(b) Illustrate how the problems in Class-B push-pull amplifier are solved in complementary symmetry Class-B amplifier. 6
14. (a) Explain the operation of Op-Amp as a comparator. 4
(b) Explain the operation of full wave rectifier with a neat circuit diagram. 6
15. (a) Explain the operation of Op-Amp summing amplifier with three inputs. 6
(b) Mention any four applications of integrator. 4
16. (a) Explain the operation of first order butter worth high pass filter using Op-Amp. 6
(b) Design a low pass filter using Op-Amp at a cut-off frequency of 1 kHz with a pass gain of 2. 4
17. Explain the need and working of instrumentation amplifier with a neat circuit diagram. 10
18. (a) Describe the working of RC integrator circuit. 5
(b) List any five applications of clamper circuit. 5
19. (a) Explain the operation of RC phase shift oscillator circuit. 6
(b) Determine the frequency of Colpitt's oscillator using $C_1 = 150$ pf, $C_2 = 1.5$ nf and $L = 50$ mH, also sketch Colpitts oscillator circuit using BJT. 4
-