Code: 15EC33T

|          | 4 ' |
|----------|-----|
| Register |     |

## III Semester Diploma Examination, April/May-2019

## ANALOG COMMUNICATION

| ANALOG COMMUNICATION   |                                       |  |
|--|---------------------------------------|--|
| Time: 3 Hours]   | Marks: 100                            |  |
| Instructions: (i) Answer any six questions from Part – A. $(5 \times 6 = 30 \text{ mark})$<br>(ii) Answer any seven full questions from Part – B. $(7 \times 10 =$ | ks)<br>70 marks)                      |  |
| PART - A   | 5                                     |  |
| 1. State and explain Thevenin's theorem with an example. FOXY ORO  |                                       |  |
| 2. State and prove superposition theorem.  | 5                                     |  |
| 3. Classify the attenuators.   | 5                                     |  |
| 4. List the characteristics of series resonant circuit.  | 5                                     |  |
| 5. Define the following:   |                                       |  |
| (i) Reflection coefficient   | · · · · · · · · · · · · · · · · · · · |  |
| (ii) Standing Wave Ratio   | 5                                     |  |
| 6. Mention the different types of transmission lines.  | 5                                     |  |
| 7. Compare Ground Wave, Sky wave and Space wave propagation.   | 5                                     |  |
| 8. Write a short note on 'Parabolic Reflector'.  | 5                                     |  |
| 9. Draw the block diagram of an electronic communication system and exp  | olain. 5                              |  |

1 of 2

## PART - B

10. Find the current through 20  $\Omega$  resistor using superposition theorem.

 $\begin{array}{c|c}
 & & & \\
 & & & \\
\hline
 & &$ 

11. Find the current through  $10 \Omega$  resistor by Thevenin's Theorem.

 $\begin{array}{c|c}
4\Omega & 5\Omega \\
+ & 20\Omega & 10\Omega
\end{array}$ 

12. Derive an expression for antiresonant frequency for RLC circuit.

10

10

10

- 13. Design a constant 'K' type  $\pi$  section high power filter having characteristic impedance of  $R_0 = 1 \text{ k}\Omega$  and cut off frequency  $f_c = 5 \text{ kHz}$ .
- 14. (a) Draw the electrical model of a transmission line and indicate the primary constants.
  - (b) List the applications of transmission lines.

5

5

15. Explain the line of sight propagation with a neat sketch.

- 10
- 16. Define demodulation. Explain linear diode detector with suitable sketch.
- 10

17. Define modulation. Explain the need for modulation.

10

18. Define AM & FM. Compare both AM & FM.

- 10
- Explain the working of a Ratio detector with suitable circuit diagram. Explain how amplitude limiting is achieved.